

BT-1/D-24

41066

BASIC ELECTRICAL ENGINEERING

Paper-B24-ESC-104

Time Allowed : 3 Hours]

[Maximum Marks : 70

Note : All questions are compulsory. The question carrying ten marks in each unit shall have a choice in attempting any one of the one option.

UNIT-I

1. Convert a set of delta connected equal resistors (each value R) into equivalent star configuration. (CO1) 2½
2. Define the Maximum Power Transfer Theorem and mathematically deduce its condition. (CO1) 5
3. Find Norton's equivalent of Circuit shown in Fig.-1 (below), w.r.t. the load resistor of 5 Ω.

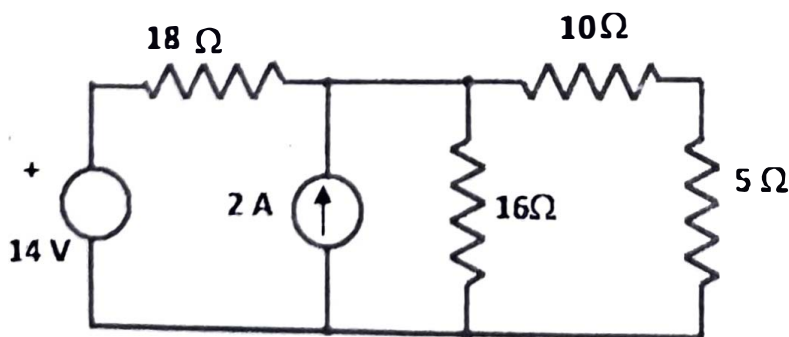


Fig-1

41066/K/1072/550

P. T. O.

Or

Find Thevenin's equivalent of ckt. Shown in Fig.-1 (above),
w.r.t the load resistor of $10\ \Omega$. (CO1) 10

UNIT-II

4. The Voltage applied to an AC circuit is $500\sqrt{2} \sin(500\pi t)$ volts and the Circuit draws a current of :

$20\sqrt{2} \sin\left(500\pi t + \frac{\pi}{4}\right)$ ampere. Taking voltage as the reference phasor, find its frequency, power factor, active power, reactive power, apparent power. (CO2) 2½

5. Given in volts : (CO2) 5

$$V_1 = 50 \sin \omega t, V_2 = 100 \sin(\omega t + 135^\circ), \\ V_3 = 200 \sin(\omega t - 135^\circ).$$

Find $V = V_1 + V_2$ in sinusoidal periodic form.

6. Explain in detail the theory of AC input response of series R-C ckt. with deducing voltage-impedance-power triangle, average power and with drawing neat waveforms of instantaneous values of voltage, current and power on simultaneous time-axis.

Or

Explain in detail the theory of AC input response of series R-L ckt. with deducing voltage-impedance-power

triangle, average power and with drawing neat waveforms of instantaneous values of voltage, current and power on simultaneous time-axis. (CO2) 10

UNIT-III

7. Draw a neat labelled diagram and Equivalent circuit of a single phase transformer. (CO3) 2½
8. Deduce the expression between line and phase voltages for a balanced for a balanced star 3-phase system. (CO3) 5
9. On a single phase transformer, explain the following :
 - (a) Open circuit test.
 - (b) Short circuit test.

Or

Explain in detail the two wattmeter method of Power measurement for a Delta connected load (any type) with suitable steps containing ckt. equations, neat phasor and ckt. diagram. (CO3) 10

UNIT-IV

10. Give functions of an armature coil in case of Generator and Motor. (CO4) 2½
11. Explain one method of speed control of a DC shunt motor and suitable ckt. diagram. (CO4) 5

41066/K/1072/550

3

P. T. O.

12. Explain with sketches the construction and working of a DC generator with commutator working.

Or

Taking X-axis intervals of 30 degrees each, draw neatly the waves on simultaneous axis : (CO4) 10

$$V_1 = V_m \sin \omega t, V_2 = V_m \sin(\omega t - 120^\circ) \text{ \&}$$

$$V_3 = V_m \sin(\omega t - 240^\circ).$$

Hence, with neat sketches, explain and prove the statement : 'A 3 phase pulsating magnetic flux produced by 3-phase excited stator winding is equivalent to a single (bipolar) rotating flux'. Hence, briefly explain how the rotor of a squirrel cage type 3-phase induction Motor starts rotating?